

$$4.7 \quad (a.) \quad Z = \frac{Z_A}{2Z_A + Z_B} \begin{bmatrix} (Z_A + Z_B) & Z_A \\ Z_A & (Z_A + Z_B) \end{bmatrix}$$

$$Y = \frac{1}{Z_A Z_B} \begin{bmatrix} (Z_A + Z_B) & -Z_A \\ Z_A & (-Z_A + Z_B) \end{bmatrix}$$

$$(b.) \quad Z = \frac{1}{Y_A Y_B} \begin{bmatrix} (Y_A + Y_B) & Y_A \\ Z_A & (Y_A + Y_B) \end{bmatrix}$$

$$Y = \frac{Y_A}{2Y_A + Y_B} \begin{bmatrix} (Y_A + Y_B) & -Y_A \\ -Y_A & (Y_A + Y_B) \end{bmatrix}$$

$$4.9 \quad V_1^+ = 14.1 \angle 45^\circ \quad V_1^- = 14.1 \angle -45^\circ$$

$$V_2^+ = 2.83 \angle -45^\circ \quad V_2^- = 2.83 \angle -135^\circ$$

$$Z_{in,1} = 50 \angle -90^\circ \quad Z_{in,2} = 50 \angle -90^\circ$$

$$4.10 \quad (a.) \quad S = \begin{bmatrix} 0 & e^{-j\beta l} \\ e^{-j\beta l} & 0 \end{bmatrix}$$

$$(b.) \quad S = \begin{bmatrix} \frac{3(1 - e^{-j2\beta l})}{9 - e^{-j2\beta l}} & \frac{8e^{-j2\beta l}}{9 - e^{-j2\beta l}} \\ \frac{8e^{-j2\beta l}}{9 - e^{-j2\beta l}} & \frac{3(1 - e^{-j2\beta l})}{9 - e^{-j2\beta l}} \end{bmatrix}$$

4.16 (a.) Network is not lossless

(b.) Network is reciprocal

(c.) $RL = 20$ dB

(d.) $IL = 8.0$ dB

(e.) $\Gamma = 0.19 \angle 90^\circ$

$$4.18 \quad S = \begin{bmatrix} \frac{Z_{o2} - Z_{o1}}{Z_{o1} + Z_{o2}} & \frac{2\sqrt{Z_{o1}Z_{o2}}}{Z_{o1} + Z_{o2}} \\ \frac{2\sqrt{Z_{o1}Z_{o2}}}{Z_{o1} + Z_{o2}} & \frac{Z_{o1} - Z_{o2}}{Z_{o1} + Z_{o2}} \end{bmatrix}$$

$$4.21 \quad Z = \begin{bmatrix} -jZ_o \cot \beta l & -jZ_o \csc \beta l \\ -jZ_o \csc \beta l & -jZ_o \cot \beta l \end{bmatrix}$$

$$4.24 \quad V_L = 1 \angle -90^\circ \text{ V}$$

$$4.30 \quad \frac{P_2}{P_1} = \frac{|S_{12}|^2 (1 - |\Gamma_2|^2)}{|1 - S_{23}^2 \Gamma_2 \Gamma_3|^2 - |S_{12}^2 \Gamma_2|^2}$$

$$\frac{P_3}{P_1} = \frac{|S_{12}|^2 |S_{23}|^2 |\Gamma_2|^2 (1 - |\Gamma_3|^2)}{|1 - S_{23}^2 \Gamma_2 \Gamma_3|^2 - |S_{12}^2 \Gamma_2|^2}$$