

Optimizing Delay

- Optimizing delay can be broken into two categories
 - Gate Size selection
 - Transistor sizing
- Gate size selection is done in a standard cell design approach in which you have a library that offers multiple drive strength cells and pick the cells sizes that give the highest speed for a design
 - Current synthesis tools do a good job
- Transistor sizing is done in a custom design in which you size individual transistors during the design process to optimize delay
 - quality depends on individual designer
 - some synthesis help available
 - simulation iteration a tempting option but can be time consuming

Gate Size Selection

- Many algorithms for gate size selection exist
- One iterative approach is known as the *Tilos* algorithm


Assumptions:

1. Can compute the delay along a path of gates
2. Have multiple gate sizes to choose from

Will yield good results for a path delay


Tilos Algorithm

 Step #1: Start with Minimum gate sizes, set *current_gate* equal to last gate, *driving_gate* to *current_gate* - 1.




Measure delay, call this *last_delay*.

 Step #2a: Increment size of *current_gate*, compute *delay_a*



Tilos Algorithm (cont.)

 Step #2b: Restore *current_gate* size. Increment size of *driving_gate*, compute *delay_b*



Step #3: Compare delays A, B against *last_delay*. Whichever shows the greatest improvement, use this new gate configuration and set *last_delay* equal to the new delay.


Repeat Steps #2, #3 until no further delay improvement.

Set *current_gate* to *driving_gate*, *driving_gate* to *current_gate-1* and repeat until all gates sized (an exception: the first gate size is considered a FIXED size as in an input buffer).

Some Observations

To save execution time, do have to compute entire path delay.

 Computing changes in delay in a 'window' around sized-gate



Compute delay changes here

Also, gate sizes do not have to be exact to get near optimum delay. If optimum gate size happens to be 2.5x, a choice of 2X or 3X will yield good results. This means that rough estimation of gate sizes or transistor sizes can often be satisfactory.

Rules of Thumb

- Keep fan-in low to keep #transistors in series low (for sub-micron, often ≤ 3).
- Keep fan-out < 5
- Along a critical path, the minimum delay is achieved if each stage delay is about equal
- Keep rise/fall times about equal

Estimating Gate Delay, Transistor sizing

- Would be nice to have a “back of the envelope” method of sizing gates/transistors that would be easy to use and would yield reasonable results
- Sutherland/Sproull/Harris book “Logic Effort: Designing Fast CMOS Circuits” introduces a method called “Logical Effort”
- Chapter 1 of the book is posted on the Morgan-Kaufman website (www.mkp.com, search for author names)
 - Download this chapter, READ IT!
- We will attempt to apply this method during the semester to the circuits that we will look at.
- Will look at static CMOS application first (these notes taken from that chapter).

Gate Delay Model

Delay will always be normalized to dimensionless units to isolate effects of fabrication process

$$d_{\text{abs}} = d * \tau$$

Where τ (Tau) is the delay of a minimum sized inverter driving an identical inverter with *no parasitics*. Tau is NOT the no-load delay of an inverter. Also, it is not the delay of a 1x inverter driving a 1x inverter since this includes the delay contributions due to parasitics.

Delay of a logic gate is composed of the delay due to *parasitic delay p* (no load delay) and the delay due to load (*effort delay* or *stage effort f*)

$$d = f + p$$

Logical effort, Electrical Effort

The *stage effort* f (delay due to load) can be expressed as a product of two terms:

$$f = g * h$$

So delay is

$$\begin{aligned} d_{\text{abs}} &= (f + p) * \tau \\ &= (g*h + p) * \tau \end{aligned}$$

g captures properties of the logic gate and is called the *logical effort*.

h captures properties of the load and is called the *electrical effort*.

RC model versus Logical Effort Model

On the surface, this does not look different from the model discussed earlier:

Logical Effort:

$$d_{\text{abs}} = (g * h + p) * \tau$$

Previous RC model


$$\text{Gate delay} = K * \text{Cload} + \text{no-load delay}$$

Where K represented the pullup/pulldown strength of the PMOS/NMOS tree.

It would help to see how the RC model can be used to derive the logical effort model.

Derivation of Logical Effort Equations via RC model

Logic Gate Model

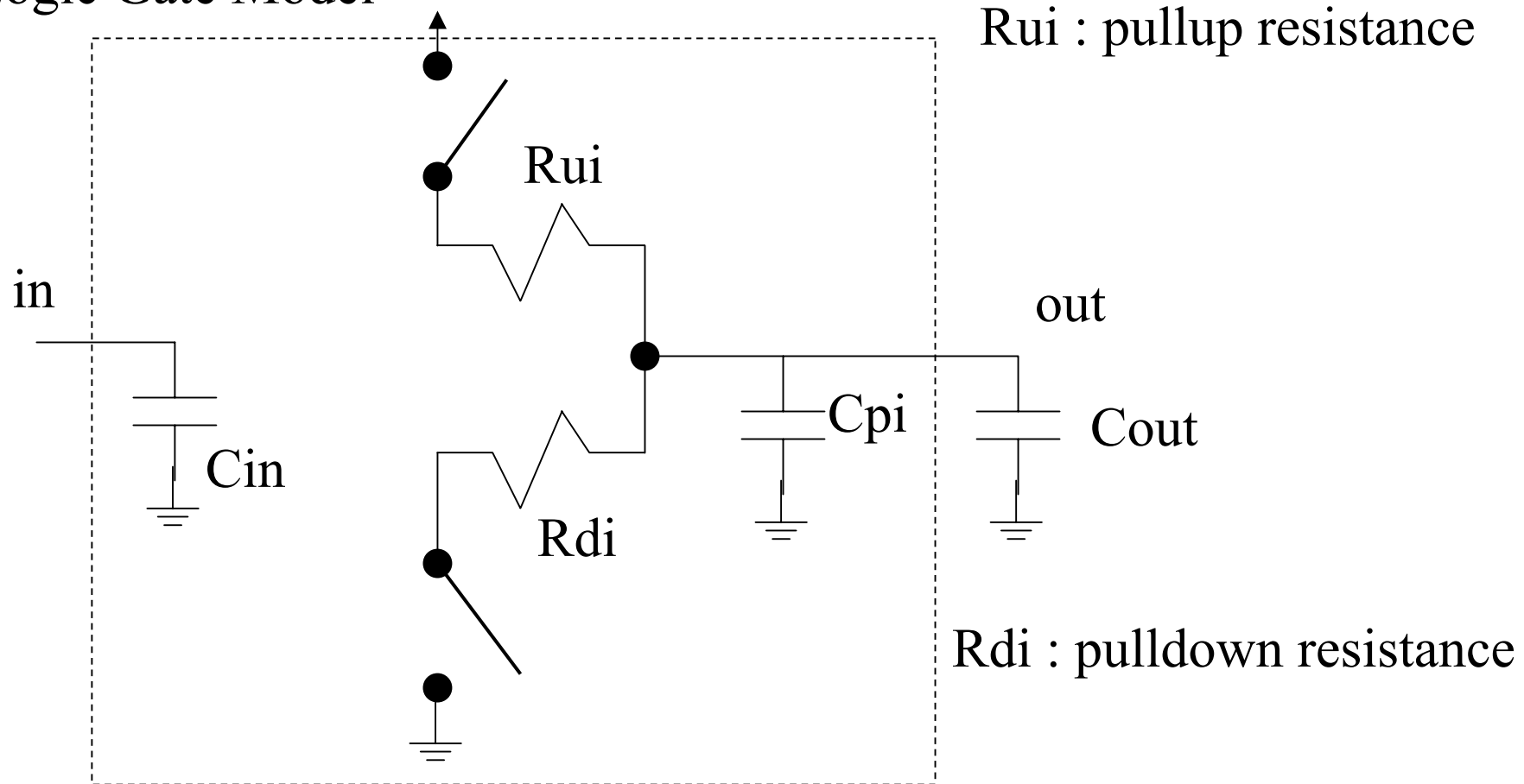

C_{pi} : parasitic cap of gate

Tau

Tau (τ) is the absolute delay of a 1x inverter driving a 1x inverter *with no parasitics*. We assume equal pullup/pulldown R_{inv} , and $C_{in} = C_{inv}$, so:

$$\text{Tau} = \kappa * R_{inv} * C_{inv}$$

where κ is a constant characteristic of the fabrication process that relates RC time constants to delay.

Note: Tau is NOT the no-load delay of an inverter. Also, it is not the delay of a 1x inverter driving a 1x inverter since this includes the parasitic delay! This means that determination of Tau cannot be done via one delay measurement.

Template Circuit

A template circuit is chosen as the basis upon which other gates are scaled. The scaling factor is α .

C_t is the input cap of the template.

R_t is the pullup or pulldown resistance of the template.

C_{pt} is the parasitic capacitance of the template.

$$C_{in} = \alpha * C_t$$

input cap scales up

$$R_i = R_{ui} = R_{di} = R_t / \alpha$$

channel resistance scales down

$$C_{pi} = \alpha * C_{pt}$$

parasitics scale up

RC Delay

$$\begin{aligned} D_{abs} &= \kappa R_i (C_{out} + C_{pi}) \\ &= \kappa (R_t / \alpha) C_{in} (C_{out} / C_{in}) + \kappa (R_t / \alpha) (\alpha C_{pt}) \\ &= (\kappa R_t C_t) (C_{out} / C_{in}) + \kappa R_t C_{pt} \end{aligned}$$

Written in this form, can see relation to logical effort model:

$$D_{abs} = \tau (gh + p)$$

$$\tau = \kappa R_{inv} C_{inv} \quad (\text{previous definition})$$

$$g = (R_t C_t) / (R_{inv} C_{inv}) \quad \text{Note: if template} = 1X \text{ inverter, then } g = 1 \text{ !!!!}$$

$$h = C_{out} / C_{in}$$

$$p = (R_t C_{pt}) / (R_{inv} C_{inv})$$



Note: book value of $P_{inv} = 1$ only true if C_{pt} (parasitics) = C_{inv} (C_{gate})!!

Logical Effort (g)


In the Sutherland/Sproull model, the logical effort g factor is normalized to a minimum sized inverter for static CMOS.

So g for an inverter is equal to 1.

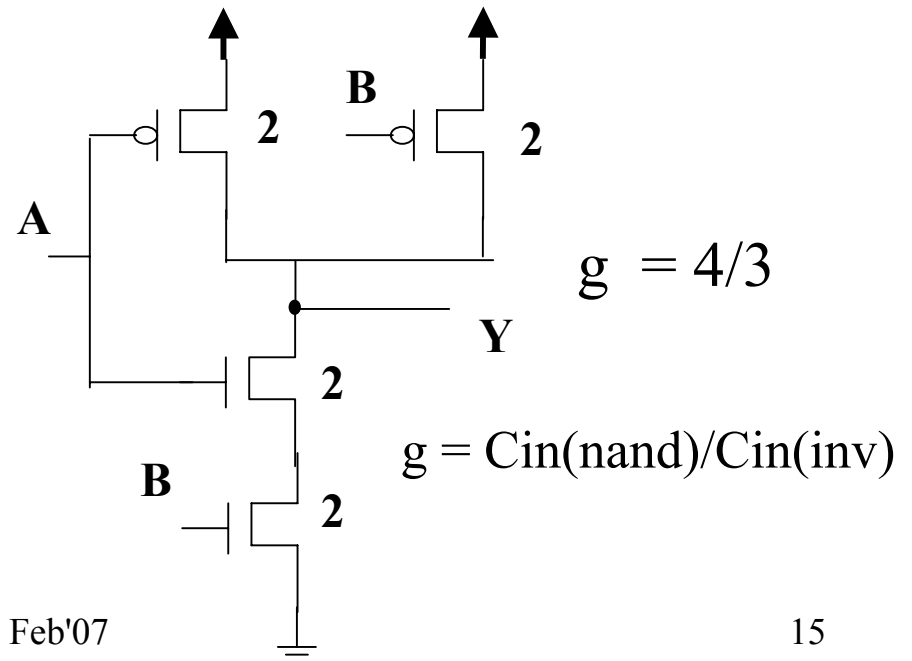 Logical effort g of other gates represents how much more input capacitance a gate must present to produce the *same output current* as the inverter (the template gate)




Logical Effort inverter vs nor2

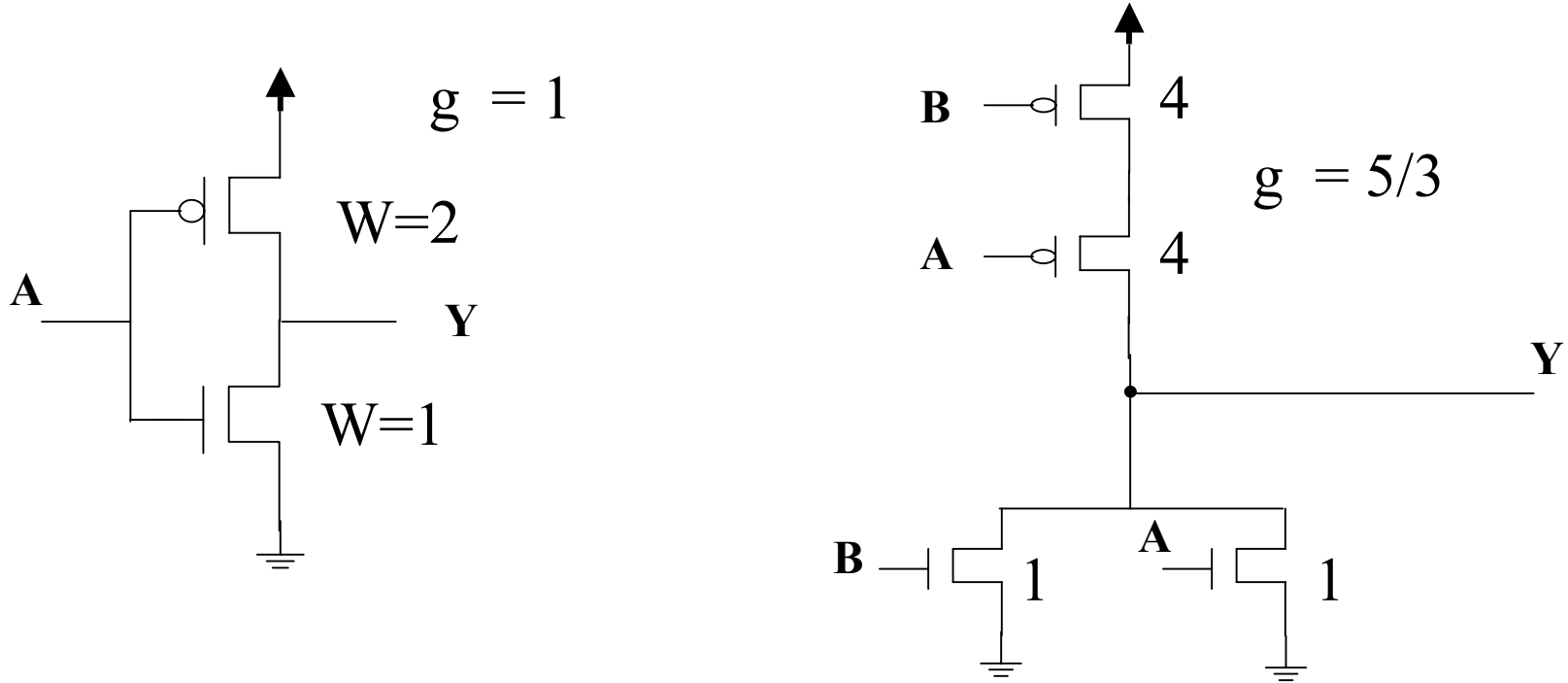


Intuitive result, Nor2 g is higher than Nand2 g

Logical Effort inverter vs Complex gate

 

$$g(a) = 4/3$$

$$g(b,c) = 2$$

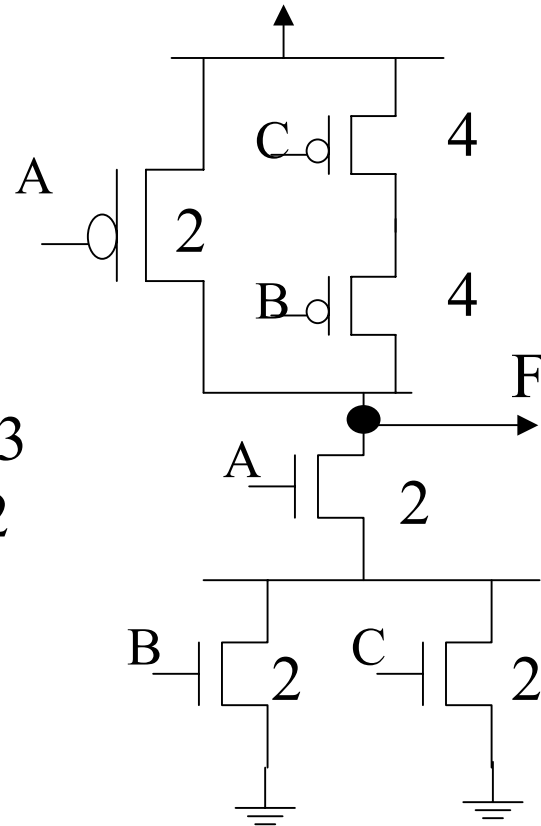

Intuitive result, worse case g of complex gate higher than Nand2 or Nor2.

In general, more inputs, more series transistors, the higher the g value.


Logical Effort vs. Electrical Effort

- The value for logical effort g depends on what gate is chosen as the template gate ($g=1$)
 - Choosing a different template gate will alter ‘ g ’ values for the other gates in your library
- The g value captures the effects of varying number of inputs, and transistor topology on more complex gates than your template gate
- More complex gates will require more logical effort to produce the same output current as the template gate, and will also present a higher input load
- The logical effort for a 1x Nand2, 2X Nand2, 4X Nand2 are all the same – the effect of the extra load by the larger transistors is captured by the *electrical effort parameter*

Logical Effort vs. Electrical Effort


- The electrical effort h parameter is used to capture the driving capability of the gate via transistor sizing and also the effect of transistor sizes on loading
- Electrical effort h is defined as
$$C_{out} / C_{in}$$
where C_{out} is the load capacitance, C_{in} is the input capacitance of the gate.
- Note that h for a gate will reduce as the transistors become wider since C_{in} increases (C_{out} is assume fixed).

Measuring P and Tau

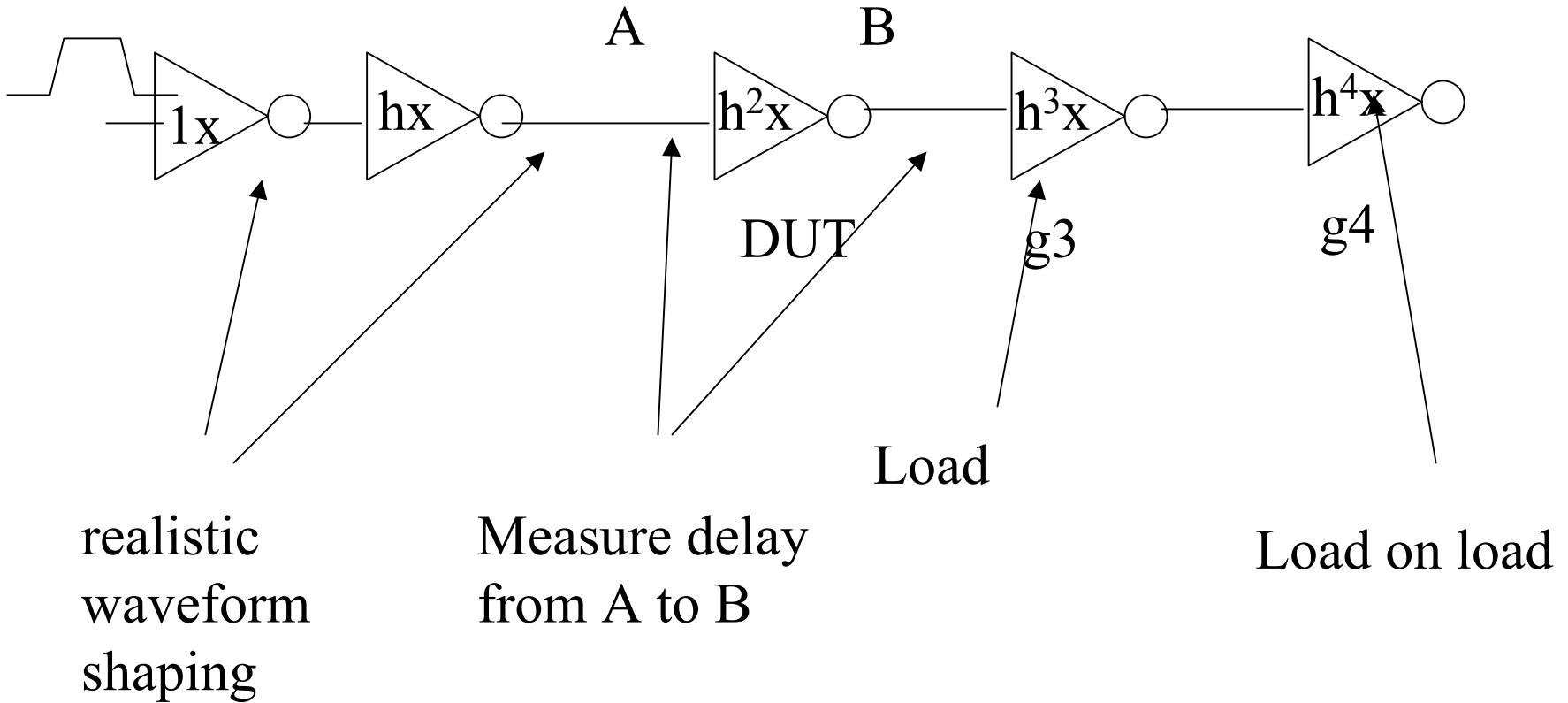

Effort at each stage is 'h'. Scaling 'h' at each level helps to keep the transition times seen by the DUT consistent

 Plot Delay, Fit to Straight line (delay = mX + b)



Tau, Pinv

By definition, $g_{inv} = 1.0$

$$\begin{aligned}\text{delay absolute} &= \tau (g \cdot h + P_{inv}) \\ &= \tau * g * h + \tau * P_{inv}\end{aligned}$$

Since $g=1$ for inverter, then:

$$\text{delay absolute} = \tau * h + \tau * P_{inv}$$

So τ = slope of the line.

Once τ is known, can calculate P_{inv} at any point as:

$$P_{inv} = (\text{Delay absolute})/\tau - h$$

Look in Harris/Weste textbook, Chapter 5, Section 5.5.3 (logical effort) for some typical values for different technologies

Measuring Logical Effort for other Gates

When replace all gates in test circuit with Nand2, and plot:

$$\text{delay} = M_{\text{nand2}} * h + P_{\text{nand2}}$$

versus

$$\text{delay} = M_{\text{inv}} * h + P_{\text{inv}}$$

the ratio of $M_{\text{nand2}}/M_{\text{inv}}$ is the logical effort of the Nand2.

Note that $M_{\text{inv}} = \tau$, so this is M_{nand2}/τ

Parasitic Delay of Other Gates

- Normalizing the parasitic delay to that of the inverter can be useful for normalization purposes.
- Some typical values according to Southerland/Sproull:


inverter $p_{\text{inv}} = 1.0$

N-input nand $n^* p_{\text{inv}}$


N-input nor $n^* p_{\text{inv}}$

Will use these values for example purposes.

Delay Estimation

 
 
$$\begin{aligned} A_delay &= g*h + p = 1*(CinB/CinA) + 1 \\ &= 1*(4*CinA/CinA) + 1 = 4 + 1 = 5 \text{ time units} \end{aligned}$$




$$\begin{aligned} A_delay &= g*h + p = (4/3)*(CinB/CinA) + 2*1 \\ Cin_B &= 4*3 = 12. \quad Cin_A = 4 \\ A_delay &= (4/3)*(12/4) + 2 = 4 + 2 = 6 \text{ units} \end{aligned}$$

Nand2 worse because of higher parasitic delay than inverter.

Note that $g*h$ term was same for both because NAND2 sized to provide same current drive.

MultiStage Delay

 - Recall rule of thumb that said to balance the delay at each stage along a critical path
- Concepts of logical effort and electrical effort can be generalized to multistage paths




$$\text{Path logical effort} = g_1 * g_2 * g_3 * g_4$$

In general, Path logic effort $G = \prod g(i)$

$$\text{Path electrical effort } H = C_{out} / C_{in_{\text{first_gate}}}$$

Must remember that electrical effort only is concerned with effect of logic network on input drivers and output load.

Off Path Load

 

Off path load will divert electrical effort from the main path, must account for this. Define a *branching effort* b as:

$$b = (\text{Con}_{\text{path}} + \text{Coff}_{\text{path}}) / \text{Con}_{\text{path}}$$

The branching effort will modify the electrical effort needed at that stage. The branch effort B of the path is:

$$B = \prod b(i)$$

Path Effort F

Path effort F is:

$$\begin{aligned} F &= \text{path logic effort} * \text{path branch effort} * \text{path electrical effort} \\ &= G * B * H \end{aligned}$$

Path branch effort and path electrical effort is related to the electrical effort of each stage:

$$B * H = C_{out}/C_{in} * \prod b(i) = \prod h(i)$$

Our goal is choose the transistor sizes that effect each stage effort $h(i)$ in order to minimize the path delay!!!!!!!

Minimizing Path Delay

The absolute delay will have the parasitic delays of each stage summed together.

However, can *focus on just Path effort F* for minimization purposes since parasitic delays are constant.

For an N-stage network, *the path delay is least when each stage in the path bears the same stage effort.*

$$f(\min) = g(i) * h(i) = F^{1/N}$$

Minimum achievable path delay

$$D(\min) = N * F^{1/N} + P$$

Note that if N=1, then $d = f + p$, the original single gate equation.

Choosing Transistor Sizes

Remember that the stage effort $h(i)$ is related to transistor sizes.

$$f(\min) = g(i) * h(i) = F^{1/N}$$


So

$$h(i) \min = F^{1/N} / g(i)$$

To size transistors, start at end of path, and compute:

$$C_{in}(i) = g_i * C_{out}(i) / f(\min)$$

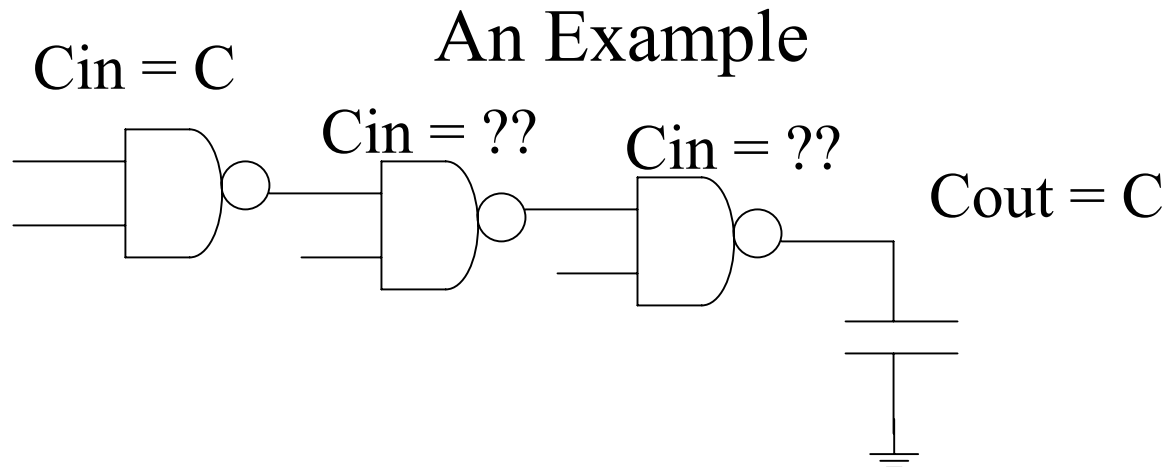Once $C_{in}(i)$ is known, can distribute this among transistors of that stage.



Size the transistors of the nand2 gates for the three stages shown.

$$\text{Path logic effort} = G = g_0 * g_1 * g_2 = 4/3 * 4/3 * 4/3 = 2.37$$

$$\text{Branching effort } B = 1.0 \text{ (no off-path load)}$$

$$\text{Electrical effort } H = C_{out}/C_{in} = C/C = 1.0$$

$$\begin{aligned} \text{Min delay achievable} &= 3 * (G * B * H)^{1/3} + 3 (2 * \text{pinv}) \\ &= 3 * (2.37 * 1 * 1)^{1/3} + 3 (2 * 1.0) = 10.0 \end{aligned}$$

An example (cont.)

The effort of each stage will be:

$$f_{\min} = (G*B*H)^{1/3} = (2.37*1.0*1.0)^{1/3} = 1.33 = 4/3$$

Cin of last gate should equal:


$$\begin{aligned} C_{in \text{ last gate (min)}} &= g_i * C_{out (i)} / f(\min) \\ &= 4/3 * C / (4/3) = C \end{aligned}$$

Cin of middle gate should equal:

$$\begin{aligned} C_{in \text{ middle gate}} &= g_i * C_{in \text{ last gate}} / f(\min) \\ &= 4/3 * C / (4/3) = C \end{aligned}$$

All gates have same input capacitance, distribute it among transistors.


Transistor Sizes for Example

 

Where gate capacitance of
 $2 * W * L$ Mosfet = $C/2$

Choose W accordingly.

Let Load = 8C, what changes?

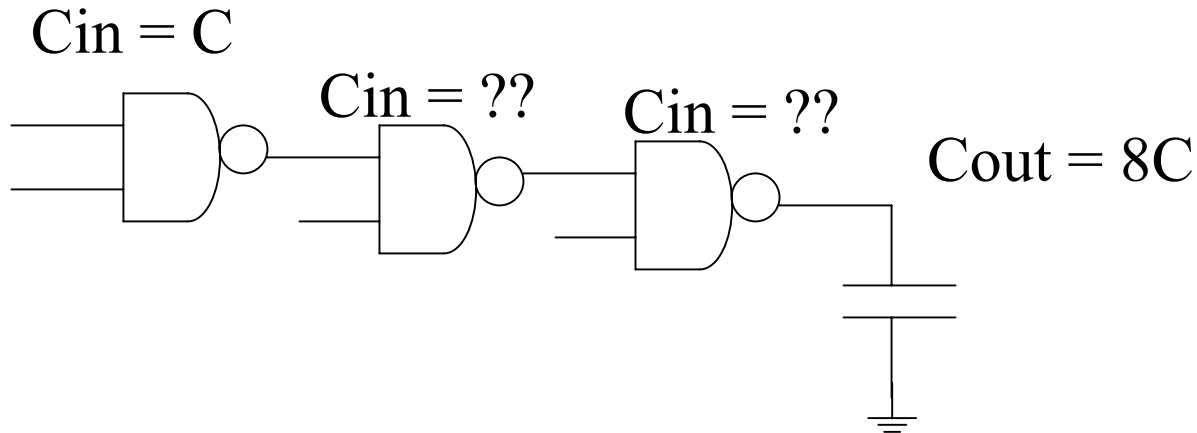

Size the transistors of the nand2 gates for the three stages shown.

$$\text{Path logic effort} = G = g_0 * g_1 * g_2 = 4/3 * 4/3 * 4/3 = 2.37$$

Branching effort $B = 1.0$ (no off-path load)

$$\text{Electrical effort } H = C_{out}/C_{in} = 8C/C = 8.0$$

$$\begin{aligned} \text{Min delay achievable} &= 3 * (G * B * H)^{1/3} + 3 (2 * p_{inv}) \\ &= 3 * (2.37 * 1 * 8)^{1/3} + 3 (2 * 1.0) = 14.0 \end{aligned}$$

8C Load Example (cont.)

The effort of each stage will be:

$$f_{\min} = (G*B*H)^{1/3} = (2.37*1.0*8)^{1/3} = 2.67 = 8/3$$

Cin of last gate should equal:


$$\begin{aligned} C_{in} \text{ last gate (min)} &= g_i * C_{out} (i) / f(\min) \\ &= 4/3 * 8C / (8/3) = 4C \end{aligned}$$

Cin of middle gate should equal:

$$\begin{aligned} C_{in} \text{ middle gate} &= g_i * C_{in} \text{ last gate} / f(\min) \\ &= 4/3 * 4C / (8/3) = 2C \end{aligned}$$

Note that each stage gets progressively larger, as is typical with a multi-stage path driving a large load.

Example 1.6 from Chapter 1

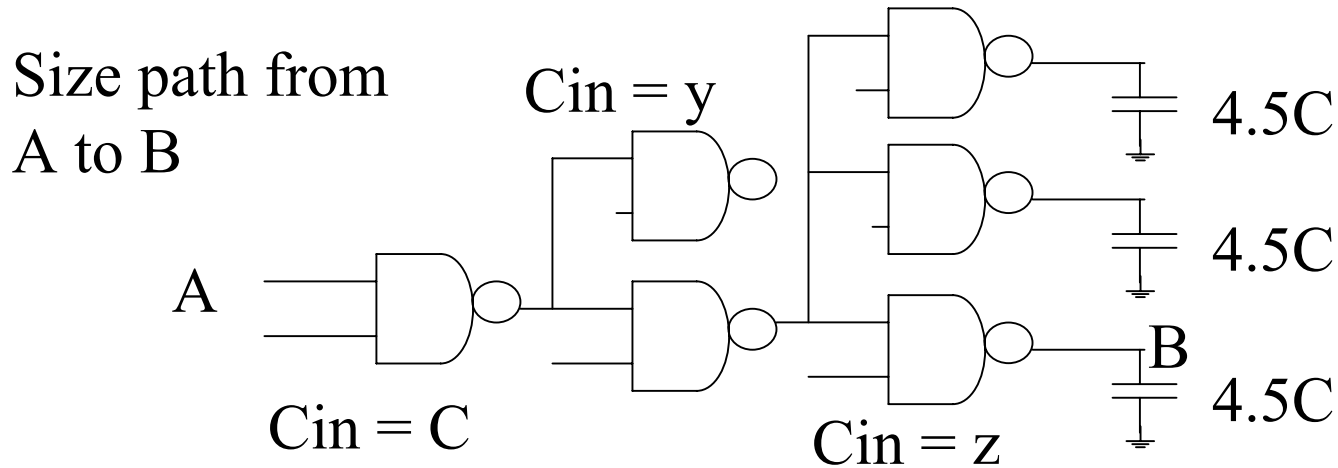

Path logic effort $G = g_0 * g_1 * g_2 = 4/3 * 4/3 * 4/3 = 2.37$

Branch effort, 1st stage = $(y+y)/y = 2$.

Branch effort, 2nd stage = $(z+z+z)/z = 3$

Path Branch effort $B = 2 * 3 = 6$.

Path electrical effort $H = C_{out}/C_{in} = 4.5C/C = 4.5$

Path stage effort = $F = G*B*H = 2.37*6*4.5 = 64$.

Min delay = $N(F)^{1/N} + P = 3*(64)^{1/3} + 3(2pinv) = 18.0$ units

Example 1.6 from Chapter 1 (cont)

Stage effort of each stage should be:

$$f(\min) = (F)^{1/N} = (GBH)^{1/N} = (64)^{1/3} = 4$$

Determine C_{in} of last stage:

$$C_{in}(z) = g * C_{out} / f(\min) = 4/3 * 4.5C / 4 = 1.5 C$$

Determine C_{in} of middle stage:

$$C_{in}(y) = g * (3 * C_{in}(z)) / f(\min) = 4/3 * (3 * 1.5C) / 4 = 1.5C$$


Is first stage correct?

$$C_{in}(A) = g * (2 * C_{in}(y)) / f(\min) = 4/3 * (2 * 1.5C) / 4 = C.$$

Yes, self-consistent.

Example 1.10 from Chapter 1

$C_{in} = 10\text{u}$ gate cap

 

Path logic effort $G = g_0 * g_1 * g_2 * g_3 = 1 * 5/3 * 4/3 * 1 = 20/9$

Path Branch effort $B = 1$

Path electrical effort $H = C_{out}/C_{in} = 20/10 = 2$

Path stage effort = $F = G * B * H = (20/9) * 1 * 2 = 40/9$

For Min delay, each stage has effort $(F)^{1/N} = (40/9)^{1/4} = 1.45$

$$z = g * C_{out}/f(\text{min}) = 1 * 20 / 1.45 = 14$$




$$y = g * C_{in}(z)/f(\text{min}) = 4/3 * 14 / 1.45 = 13$$

$$x = g * C_{in}(y)/f(\text{min}) = 5/3 * 13 / 1.45 = 15$$


Misc Comments

- Note that you never size the first gate. This gate size is assumed to be fixed (same as in the Tilos algorithm) – if you were allowed to size this gate you find that the algorithm would want to make it as large as possible.
- This is an estimation algorithm. The author claims that sizing a gate by 1.5x too big or two small still results in path delay within 5% of minimum.

Evaluating different Structure options

   

Option #1

 

Path logic effort $G = g_0 * g_1 * g_2 = 1 * 6/3 * 1 = 2$


Path Branch effort $B = 1$

Path electrical effort $H = C_{out}/C_{in} = 8C/C = 8$

Path stage effort = $F = G * B * H = 2 * 1 * 8 = 16$

$$\begin{aligned} \text{Min delay:} &= N * (F)^{1/N} + P \\ &= 3 * (16)^{1/3} + (p_{inv} + 4 * p_{inv} + p_{inv}) \\ &= 3 * (2.5) + 6 = 13.5 \end{aligned}$$

Option #2

 

Path logic effort $G = g_0 * g_1 * g_2 = 1 * 4/3 * 5/3 = 20/9$

Path Branch effort $B = 1$

Path electrical effort $H = C_{out}/C_{in} = 8C/C = 8$

Path stage effort = $F = G * B * H = 20/9 * 1 * 8 = 160/9$

$$\begin{aligned} \text{Min delay: } &= N * (F)^{1/N} + P \\ &= 3 * (160/9)^{1/3} + (p_{inv} + 2 * p_{inv} + 2 * p_{inv}) \\ &= 3 * 2.6 + 5 = 12.8 \end{aligned}$$

Option #2 appears to be better than Option #1, by a slight margin.