

## ECE3424 Electronic Circuits Laboratory


Experiment #6

Optimization of single-transistor BJT amplifiers

vers 2.4

**OBJECTIVE:** Measure transfer characteristics of a single-transistor BJT amplifiers and qualify circuit distortion in terms of the effect of the bias network of resistances.

**Background:** An amplifier is effectively represented by the two-port model of figure 6.1. The output signal is labeled as  $v_L$  because it is applied across the load  $R_L$ . The characteristics of the transfer circuit include an input resistance  $R_{in}$  and an output resistance  $R_{out}$  as well as the transfer gain  $A_V$ .

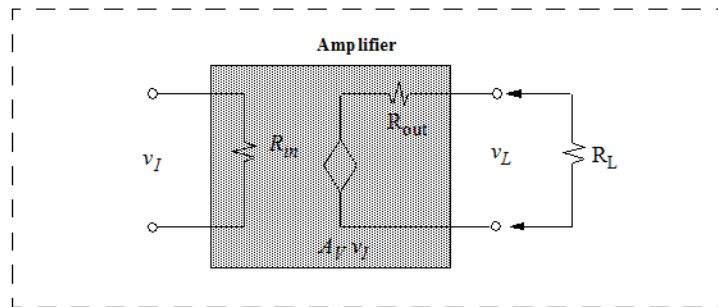


**Figure 6.1** Amplifier characteristics

These signals and amplifier transfer characteristics are all based on small increments of voltage at the input and output, for which  $\Delta V_I = v_i$ ,  $\Delta V_L = v_L$ . Consequently the input and output resistances are not just equivalent resistances but include components that are slopes. For example  $R_{in} = v_i/i_i = dV_i/dI_i$ . So measurement cannot be done by a DMM.


### PROCEDURE:

**A-1:** The amplifier topology that we will consider is by figure 6A-1. This topology is defined as the *common-emitter* (CE) configuration, and is a general-purpose amplifier topology.

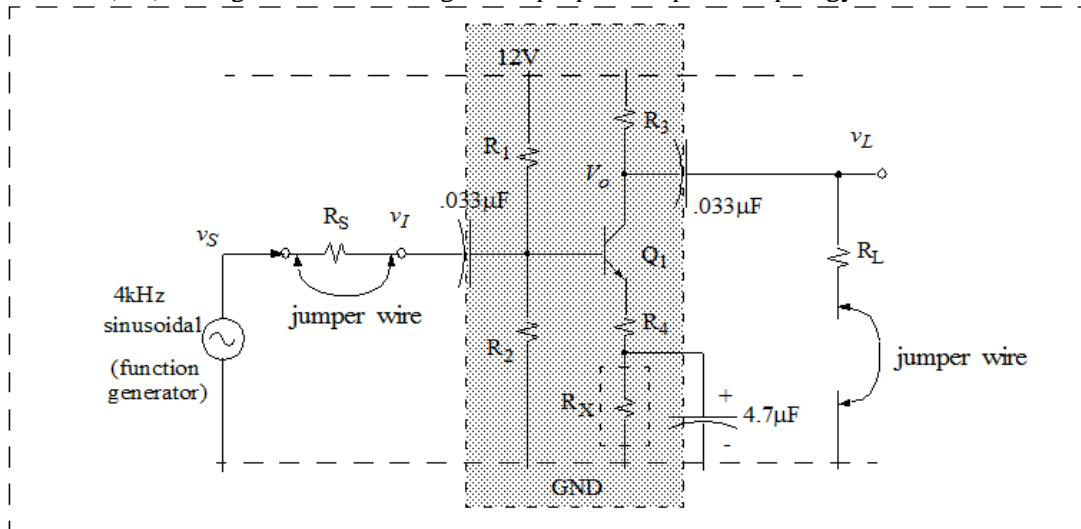

**Figure 6A-1.** Common-emitter (i.e. general purpose) configuration for test of amplifier characteristics



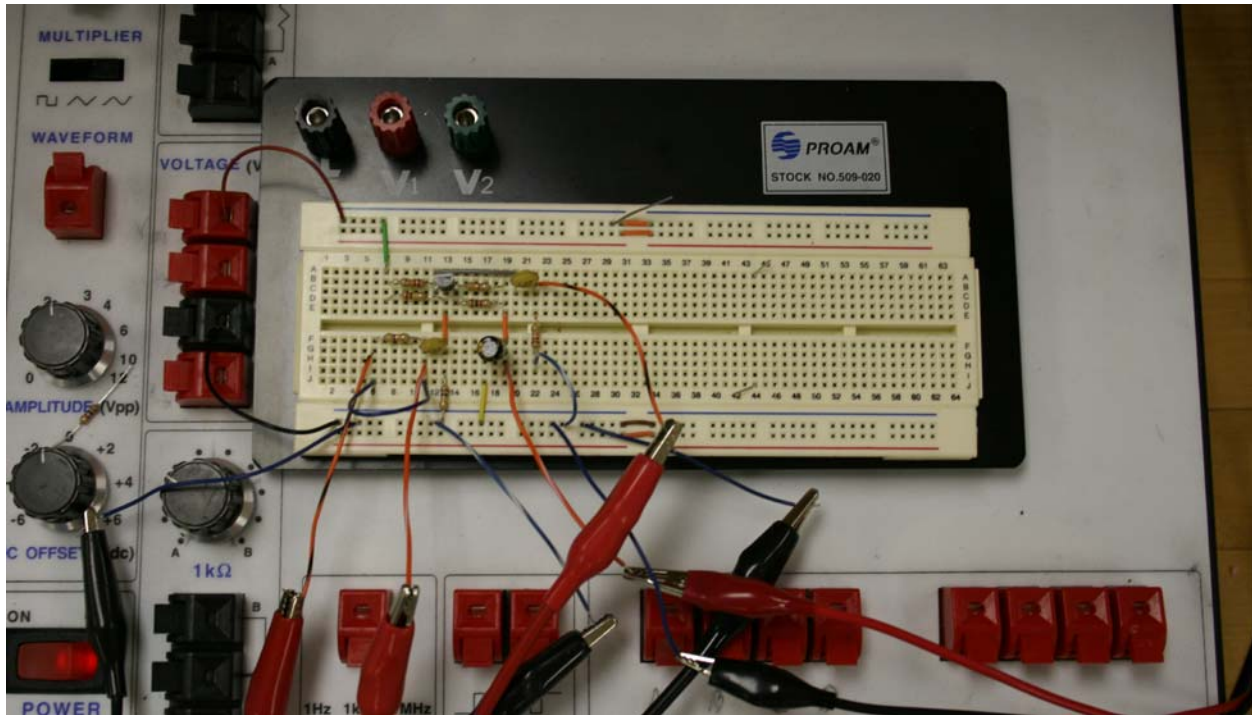

**Figure 6A-4b** Suggestions on placement and wiring. Photo.


As represented by figures 6A-4a and 6A-4b, if you lay out the circuit on the protoboard with roughly the same topology as the circuit diagram itself there is less aptitude for wiring error.

**A-3.** The reason that  $R_4$  is chosen as the parallel combination  $330\Omega || 1.0k\Omega$ , is because it is desired that  $R_4$  be switched between values of  $0.25k\Omega$  and  $1.0k\Omega$ , which is readily accomplished by pulling the  $330\Omega$  free. On the other hand resistance  $R_3$  switched between  $10k\Omega$  and  $22k\Omega$  by exchange. Load resistance  $R_L$  and source resistance  $R_S$  are switched in and out by the jumper wires, which should also be fairly visible on the placement and wiring figures.

Resistance  $R_X$  is switched between values of  $10k\Omega$  and  $50k\Omega$  by toggling the *Rbox* settings. This resistance essentially controls the current through the transistor. The detailing for which a current level is defined from  $R_X$  is left to the spreadsheet. Set it initially to  $R_X = 10k\Omega$ .

**A-4.** Once everything is wired turn on the 12V power supply and snake check the circuit by use of the DMM probes to check the voltages at the base ( $V_B$ ), emitter ( $V_E$ ) and collector ( $V_C$ ). Expect  $V_B$  and  $V_E$  to be approximately 3.6V and 2.9V respectively. Assurance that the transistor is conducting is confirmed when its node values fall between the power rails. If the transistor is not ON its node values will either be 12V or 0V.

**A-5.** Insert the jumper wires as indicated at the input and outputs. Apply a 10kHz signal with peak-peak amplitude 400mV to the input. Output peak-peak amplitude should be considerably larger than that of the input amplitude (on the order of 1.5V) but so badly distorted that it would be meaningless to make any transfer gain measurements. A typical output, with distortion, is shown by figure 6-5. If input amplitude is increased you should see the output signal distorted at both lower and upper extrema.

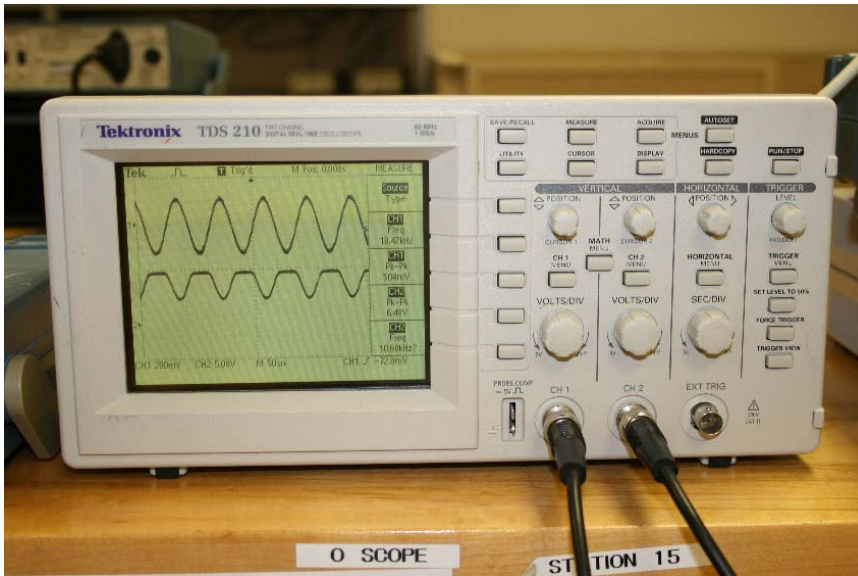


**Figure 6-5** Distortion limiting of the output signal.

**A-6.** Execute the test series shown by table A-6.1 indicating whether the output is doubly distorted or distorted at one extreme. Apply the CH2 tap to  $V_C$  rather than  $V_L$  since the output at  $V_C$  will tell you more about the origins of the distortion. Set the CH2 scope trace to ‘DC coupling’, increase the input until output distortion results at both upper and lower extrema and determine values for these distortion limits from the DC values of the scope traces. You may have to flip back and forth between ‘DC coupling’ and ‘GND’ settings of CH2 to make a relative measure between GND and the distortion (compliance) limits.

**Table A-6.1:** Test matrix and spreadsheet data table for  $f_s = 10\text{kHz}$ ,  $V_s = 400\text{mV}$  pk-pk

R3	R4	RX	Distortion (upper, lower)	Distortion limit value(s)
22k $\Omega$	250 $\Omega$	10k $\Omega$		
22k $\Omega$	250 $\Omega$	50k $\Omega$		
22k $\Omega$	1.0k $\Omega$	10k $\Omega$		
22k $\Omega$	1.0k $\Omega$	50k $\Omega$		
10k $\Omega$	250 $\Omega$	10k $\Omega$		
10k $\Omega$	250 $\Omega$	50k $\Omega$		
10k $\Omega$	1.0k $\Omega$	10k $\Omega$		
10k $\Omega$	1.0k $\Omega$	50k $\Omega$		

**B-1.** Reduce input signal level  $V_s$  (as much as possible subject to noise) until distortion is no longer evident and take measurements of  $A_v$  and  $R_{in}$  for all settings of table A-6.1. Figure B-1.1 should be a sufficient guide for these tests. The assessment of  $R_{in}$  is accomplished by measurement of  $v_L$  via the ‘measure’ button on your O-scope) with the shorting wire at the input alternately connected and disconnected. Some settings may preclude reasonable measurements because of distortion. Let the distortion tests of part A be your guide. It will probably be to your advantage to keep the output loaded by the resistance  $R_L$  for measurement of  $R_{in}$ , but you will also have to measure the output under no-load conditions (i.e.  $R_L$  disconnected) in order to determine transfer gain  $A_v$ .

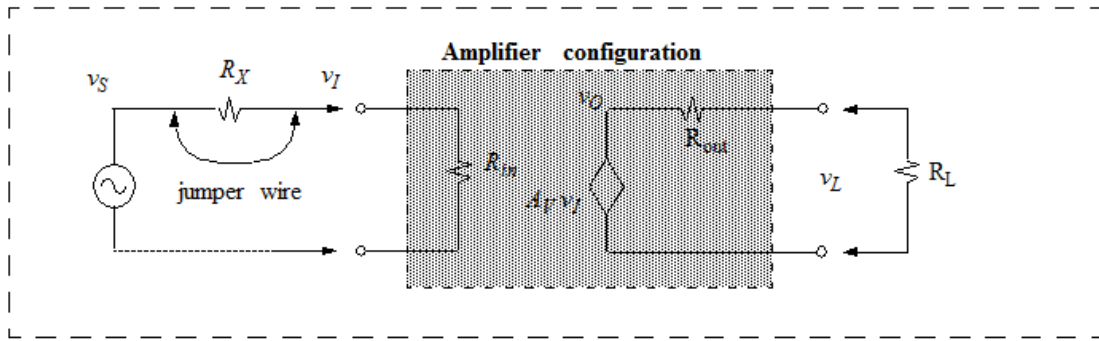


**Figure B-1.1.** Measurement of input resistance and transfer gain.

If you take the output off  $v_L$ , then  $R_{in}$  is measured by the ratio (use spreadsheet to extract  $R_{in}$ ).

$$\frac{v_L(OFF)}{v_L(ON)} = \frac{R_{in}}{R_{in} + R_X} \quad (6B-1)$$

where  $v_L(OFF)$  is with input jumper disconnected, and  $v_L(ON)$  is with input jumper connected.

**B-2.** In like manner measure the output resistance by means of the jumper wire at the output.

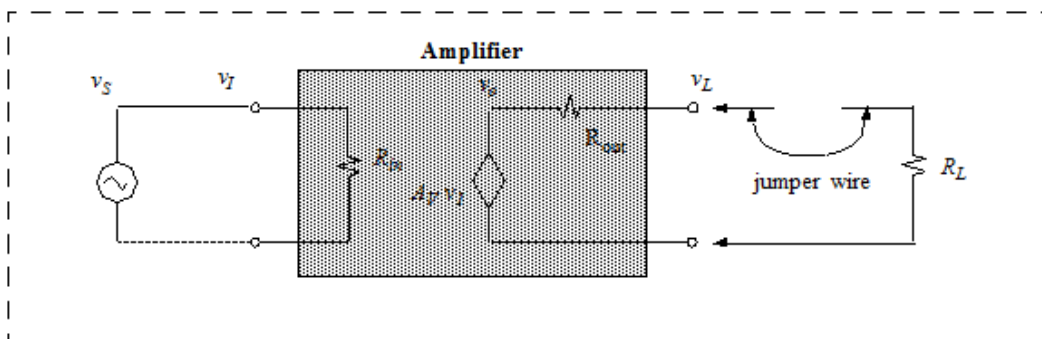

**Figure B-2.1** Measurement of output resistance.

In like manner, with measurement at output node  $v_O$  then  $R_{out}$  is measured by the ratio (use spreadsheet to determine  $R_{out}$ ).

$$\frac{v_O(ON)}{v_O(OFF)} = \frac{R_L}{R_{out} + R_L} \quad (6B-2a)$$

where  $v_L(ON)$  is with jumper to load connected, and  $v_L(OFF)$  is with jumper to load disconnected.

(variant 2): If you have inserted a resistance  $R_X$  between the output of the amplifier and the load  $R_L$ , and deployed the jumper wire across  $R_X$  then you should expect that the ratio should be a little more complicated but still viable, namely

$$\frac{v_O(ON)}{v_O(OFF)} = \frac{R_L}{R_{out} + R_L} \times \frac{R_{out} + (R_L + R_X)}{(R_L + R_X)} \quad (6B-2b)$$

and you will need more algebra to solve for  $R_{out}$  (recommend that you divide all  $R$ 's by  $R_L$ ). The spreadsheet should then do the calculation.

(variant 3): Another option is that you could have taken the output off  $v_L$ , and then used a jumper to take out  $R_X$  in like manner to variant 2 in which case the ratio is then

$$\frac{v_O(ON)}{v_O(OFF)} = \frac{R_L}{R_{out} + R_L} \times \frac{R_{out} + R_X}{R_L + R_X} \quad (6B-2c)$$

and you will need some other algebraic usage to solve for  $R_{out}$  (recommend that you divide all  $R$ 's by  $R_L$ ). (The spreadsheet should then do the calculation.)

Whatever variant is/(was) employed the result should be the same.

### ANALYSIS and REPORT:

1. The following relationships are the small-signal analytical relationships for the transfer characteristics associated with the CE (general purpose) topology:

$$R_{in} = R_1 \parallel R_2 \parallel R_{iB} \quad \text{where} \quad R_{iB} \cong \beta_F \times \left( \frac{1}{g_m} + R_4 \right)$$

$$R_{out} = R_3 \parallel r_{out} \quad \text{where} \quad r_{out} = r_o \left( \frac{\beta_F (1/g_m + R_4)}{(\beta_F / g_m) + R_4} \right)$$

$$A_V = \frac{v_L}{v_I} \cong - \frac{R_3 \parallel R_L}{1/g_m + R_4} \quad g_m = 40 \times I$$

$$\text{and} \quad I \cong (V_{BB} - 0.7)/(R_4 + R_X) \quad \text{for which} \quad V_{BB} = \frac{R_2}{R_1 + R_2} \times 12.0V$$

As an approximation we may accept defaults  $r_o = 100k\Omega$  and  $\beta_F = 100$

2. Complete your data table with columns that compare  $A_V$ ,  $R_{in}$ , and  $R_{out}$  as evaluated by the analytical relationships with the values as measured. Comment on comparisons and accuracy of measurement.

3. Use the results of your measurements to determine the best-fit value for forward current gain  $\beta_F$  of the 2n3904 transistor.

4. What are your conclusions about the effect of the resistance bias network on the compliance limits of the transfer characteristics?

5. Execute a pSPICE simulation of figure 6A-1 by means of a transient analysis for the case in which  $R_L =$  infinity,  $R_3 = 22k\Omega$ ,  $R_4 = 250\Omega$  and with  $R_X$  stepped from 10k $\Omega$  to 50k $\Omega$  in 4 steps. Compare your results with the compliance limits reflected by pSPICE to those that you determined.

In addition and concurrently to the transient analysis displays of  $V(V_L)$ , invoke a Fourier analysis (**Analysis>Transient>Enable Fourier**) for output =  $V(V_L)$  and center frequency = 10kHz with 10 harmonics. The Fourier output results will be listed as a text file under **Analysis>Examine Output**, probably toward the bottom of the file. List the THD (total harmonic distortion) for each case as part of your data analysis.

6. Design a CE general purpose amplifier (i.e. identify a complete set of bias frame resistance values  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$ , and  $R_X$ ) which makes use of a 12V supply as used by the experiment and yields a 5.0V pk-pk output at 10kHz to an  $R_L = 120\text{k}\Omega$  load with no more than 5% THD, with transfer gain  $A_V = 25\text{V/V}$  and  $R_{in} = 50\text{k}\Omega$  or larger. (Hint: Use pSPICE as a test bed and step  $R_X$ ). You will need to elect different values for all resistances, including  $R_1$  and  $R_2$ . Include a pSPICE simulation as confirmation, with schematic, and show the Fourier table (which will display the output amplitude and the THD of your design).