

Cover Sheet

Quiz #1b

Ideal opamps, pn junctions and diode circuits

$$A_{non-invert} = \frac{1}{\beta} = \frac{R_2 + R_1}{R_1}$$

$$A_{invert} = -\frac{R_2}{R_1} = -\alpha$$

Instrumentation amplifier

$$A_{IA} = \alpha \times \left(1 + \frac{2R_4}{R_3} \right)$$

Ideal diode equation: $I = I_S [e^{V/nV_T} - 1]$

Time averages of rectified sinusoidal waveforms (diode rectification)

$$\langle V(HWR) \rangle = \frac{1}{\pi} V_P \quad \langle V(FWR) \rangle = \frac{2}{\pi} V_P \quad \langle V(3\phi R) \rangle = \frac{3}{\pi} V_P$$

AC-DC converters:

$$V_{DC} = V_P - 0.5V_R$$

half-wave V_{ripple} :

$$V_R = \frac{V_P}{fR_L C} = \frac{I_L}{fC}$$

full-wave V_{ripple} :

$$V_R = \frac{V_P}{2fR_L C} = \frac{I_L}{2fC}$$

three-phase I_{ripple} :

$$I_R = 0.134I_P$$

or $V_{Ripple} = \frac{V_P}{6fR_L C}$ (with capacitance regulation)

Level shifter $\Delta V = \frac{\alpha - 1}{\alpha + 1} \times (V_P - V_D)$ where $\alpha = \frac{|V_1| - V_D}{|V_2| - V_D}$ and for which $2V_P = |V_1| + |V_2|$

If input = square wave then $\alpha = \frac{R_1}{R_2}$, if triangle wave then $\alpha = \left(\frac{R_1}{R_2} \right)^{1/2}$, if sine wave then $\alpha = \left(\frac{R_1}{R_2} \right)^{2/3}$,

Charge pump/voltage multiplier:

$$V_{out} = N \times V_C$$

$$V_C = 2(V_P - V_D)$$

$$w(\text{capacitance}) = \frac{1}{2} CV^2$$


$$T = \frac{C_Q}{C_P} \times \frac{N^2}{2f}$$

$$I_Q(\text{max}) = 2fC_P V_C$$

Instrux: Show work in space provided Be neat, concise, encircle answers Else -10 pts


If you encounter a question for which you don't know how to resolve an answer, don't sit there and flounder. Go to the next question. There are excess pts.

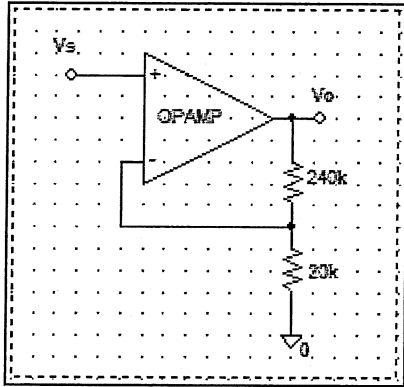OA-1 (20 pts) Assume ideal opamps and find information as indicated (by inspection, if possible).




$v_o/v_s = +13 \text{ V/V}$

$R_{in} = \infty$

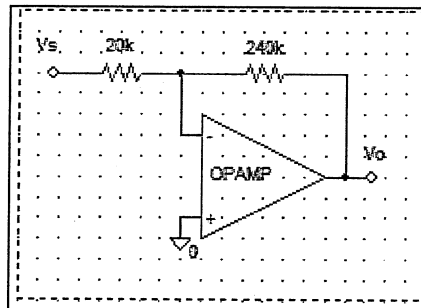


$v_o/v_s = -12 \text{ V/V}$

$R_{in} = 20 \text{ k}\Omega$

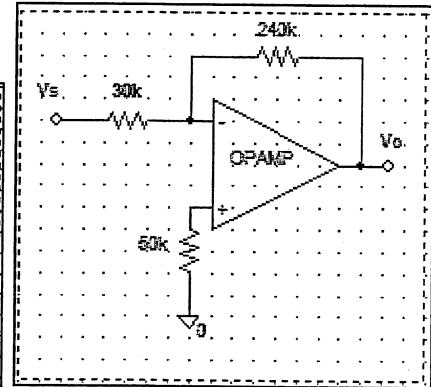


$v_o/v_s = -8 \text{ V/V}$

$R_{in} = 30 \text{ k}\Omega$

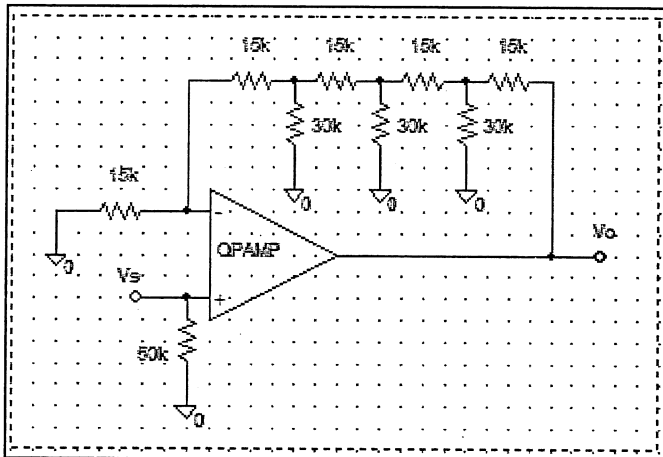

$v_o/v_s = +16 \text{ V/V}$

$R_{in} = 50 \text{ k}\Omega$

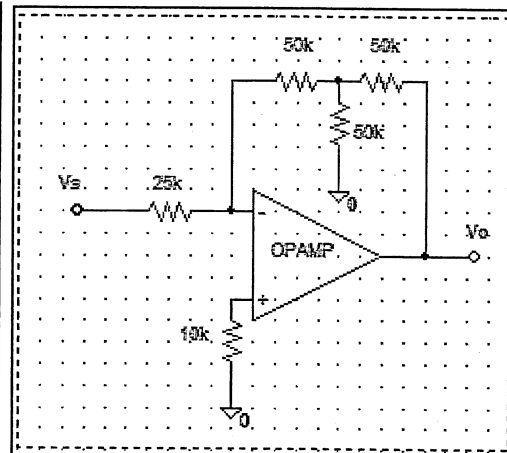


$v_o/v_s = -6 \text{ V/V}$


$R_{in} = 25 \text{ k}\Omega$

D-1. (6 pts)

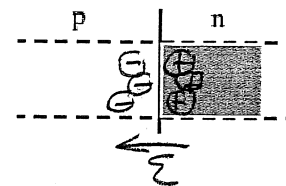Indicate on the *pn* junction figure (1) the polarity of charges (+, -) that are uncovered by the diffusion in the vicinity of the junction and (2) the direction (arrow) of the built-in E-field. Assume $V_{bias} = 0$.




D-2. (6 pts)

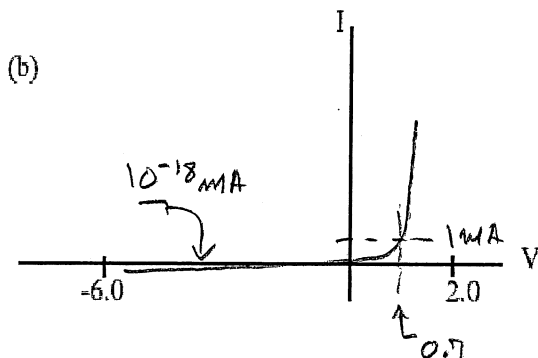

Sketch a representative plot of I vs V characteristics for the *pn* junction for bias over the range $-6.0V$ to $+2.0V$ and identify typical magnitudes of current levels I for forward and reverse biases.

D-3. (9 pts) For the diode circuit shown find the values of voltages V_3 , V_4 and current I_3 , using the constant voltage drop (CVD) model of the diode.

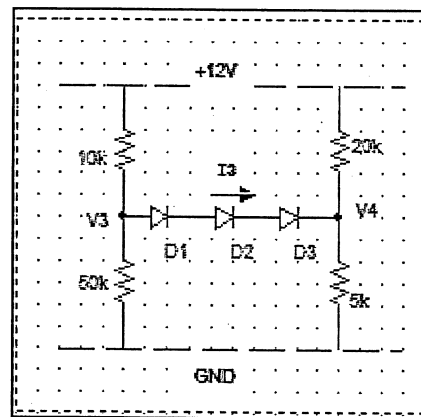Hint: Apply nodal analysis at nodes V_3 and V_4 .



$$\begin{aligned} \textcircled{V_3} \quad & V_4 + 2.1 \\ & V_3(0.1 + 0.02) - 0.1 \times 12 + I_D = 0 \\ & V_4(-0.05 + 0.2) - 0.05 \times 12 - I_D = 0 \end{aligned}$$

$$V_4(0.12 + 0.25) + 2.1 \times 0.12 - 1.8 + 0 = 0$$


0.252

$$\therefore V_4 = \frac{1.8 - 0.252}{0.37} \approx \boxed{4.18 \text{ V}}$$


$$V_3 \approx V_4 + 2.1 \approx \boxed{6.28 \text{ V}}$$

$$I_D = I_3 = \frac{V_4}{4} \times (0.25) - 0.6 = \boxed{0.446 \text{ mA}}$$

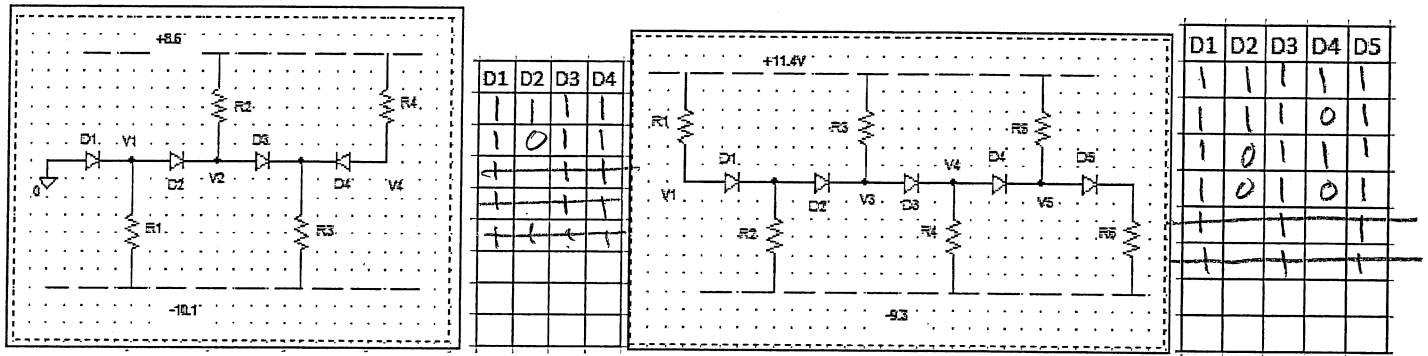D-4 (12 pts) Identify all possible active operating states for the diode circuit string as shown by their 'state tables'. Use "1" to indicate that a diode is conducting and "0" to indicate that a diode is non-conducting



D-5. (16 pts)

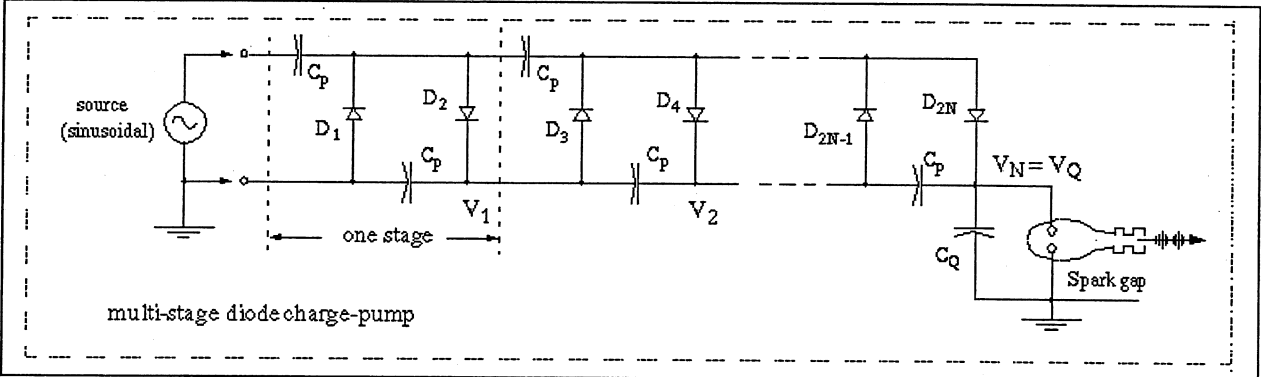

The circuit shown is to be used to ignite the plasma chamber for plasma pulse weapons located around the perimeter of a high-security residence. The charge pump capacitances C_p are all of value 250pF except for the storage capacitance C_Q , which is of value 0.1μF. The electrodes are 0.4mm apart and the breakdown field is 10,000V/cm. There are 100 stages. Find

(If you can determine any of the answers by inspection that would be OK.)

(a) What amplitude input signal is required to ignite the plasma, assuming CVD model for the diodes?

$$V_Q = 10000 \times 0.04 = 400V = \frac{1}{100} \times V_C \rightarrow = 2(V_S - V_D) \quad V_S = \boxed{2.7V}$$

(b) How much energy (Joules) is released in each plasma pulse?

$$W_Q = \frac{1}{2} \times 0.1 \mu F \times (400)^2 = \frac{1}{2} (0.1) \times 160,000 \mu J \quad w_Q = \text{energy} = \boxed{8 \text{ mJ}}$$

(c) At what frequency does the signal generator need to operate in order to charge the plasma spark capacitance (C_Q) at a rate (frequency) of 50Hz? Assume each stage requires one cycle to recharge.

$$T = \frac{1}{f} = \frac{C_Q}{C_p} \times \frac{N^2}{2f} \quad \therefore f = \frac{C_p}{C_Q} \times \frac{N^2}{2} \times \frac{1}{N} \times \frac{1}{2} \times 50$$


$$400 \times 5000 \times 50 \quad \frac{0.1 \mu F}{0.25 \mu F} \times 100^2 \times 50 \quad f = \text{freq} = \boxed{100 \text{ MHz}}$$

(d) Using the freq determined by part (c) what is the maximum current that flows forward courtesy of the charge pump action?

$$I_Q = 2f \times C_p V_C = 2 \times 100 \text{ MHz} \times 0.25 \mu F \times (2 \times (2.7 - 0.7)) I_Q = \boxed{200 \text{ mA}}$$

$$= 2 \times 100 \text{ m} \times 0.25 \times 4$$

D-6 (8 pts) Level shifter

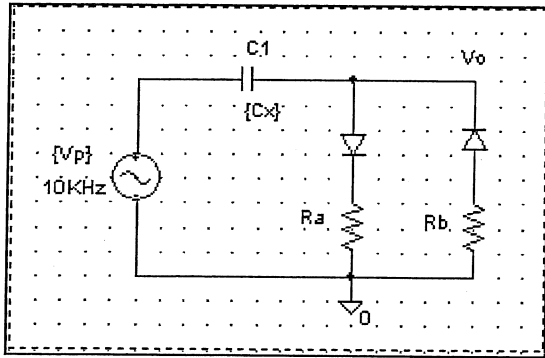


The circuit shown to the left is a level-shifter for which the input is sinusoidal $= V_p \sin(\omega t)$ where $V_p = 6.0V$. For the resistance $R_a = 300k\Omega$ and $R_b = 100k\Omega$, by how much ΔV is the shift in level at equilibrium, assuming the formula on the cover sheet? Assume $V_{diode} = V_D = 0.5V$.

$$V_{1,2} = \left(\frac{300}{100} \right)^{2/3} = 2.08$$

$$\Delta V = \boxed{1.93V}$$

$$\Delta V = (6.0 - 0.5) \times \left(\frac{2.08 - 1}{2.08 + 1} \right) = 5.5 \times 0.35 \approx +1.93V$$

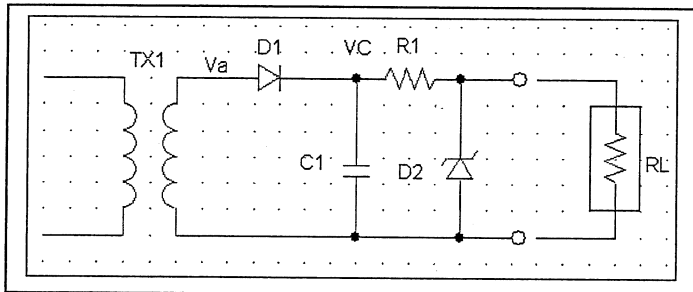D-7 (15 pts) For the HWR (half-wave rectifier) 'knob' shown, for which we desire to choose component values that will support a regulated 0.4W, 4.0V application from a 120V 60Hz source. A zener diode with $V_z = 4.0V$ is placed in the circuit as shown. Assume that transformer turns ratio n is chosen so that the peak voltage V_p across the capacitance is 10V.



(a) If $V_C(\min) = 8V$ with the load connected, what value of R_1 and of C_1 is required assuming that the current through the zener diode approaches zero when V_C approaches $V_C(\min)$. (Note that Vripple $V_R = V_p - V_C(\min)$).

(b) What average power must the zener diode dissipate when the load is not connected?

$$a) \left. \begin{array}{l} V_C(\max) = 10V \\ V_C(\min) = 8V \end{array} \right\} V_R = 2.0V = V_p / (fRC) \quad V_p = V_C(\max) = 10V$$

$$I_L = P_L / V_z = 0.4W / 4V = 0.1A, \quad R_L = 4V / 0.1A = 40\Omega$$

$$\therefore R_1 = (V_C(\min) - V_z) / I_L = (8 - 4) / 0.1 = \boxed{40\Omega}$$


$$C = \frac{V_p}{f V_R} \times \frac{1}{V_z} \times (R_1 + R_L) = \frac{10}{60 \times 2} \times \frac{1}{4} \times (40 + 40) = \boxed{1042 \mu F}$$

$$b) I_z(\min) = I_L = 0.1A = 100mA$$

$$I_z(\max) = I_1(\max) = \frac{V_C(\max) - V_z}{R_1} = \frac{10 - 4}{40} = 150mA$$

$$\therefore P_z = \frac{1}{2} (100mA + 150mA) \times \frac{V_z}{4} = \boxed{500mW}$$

A-1 (10pts) The alternator of an automobile can be represented by the circuit shown. The alternator consists of three coils, energized sequentially at phase angles that are 120° with respect to each other by the rotating electromagnet. The three phases are rectified by diodes D_1 , D_2 , and D_3 . The charging voltage applied to the battery is sampled by a control circuit which adjusts the strength of the electromagnet rotor by means of a dependent source.

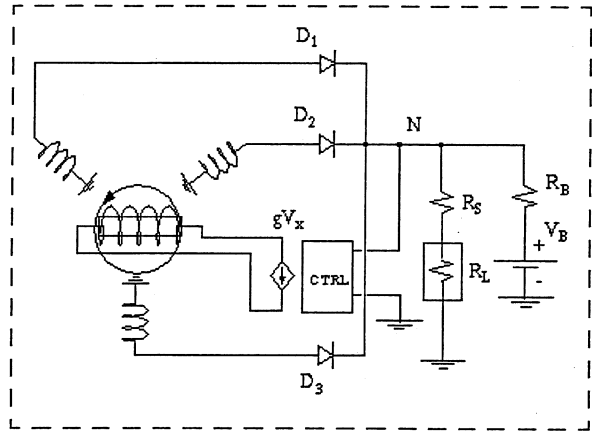

The resistance $R_B = \text{battery resistance} = 0.15\Omega$

(a) For $V_B = 12\text{V}$ determine V_N (max) at charging current 50 A and the percentage ripple in V_N that results.

(b) What drop-down resistance R_S is required for an application (shown as R_L) that uses 0.45W of power at 9.0V , and what voltage ripple V_R would occur across the application?

a) $V_N = 12 + 50 \times 0.15 = 19.5$
 $V_P = \pi/3 \times 19.5 = 20.4\text{V}$ $\Delta V = V_R = 0.134 \times V_P = 2.74\text{V}$
 Ripple = $V_R / V_P = 13.4\%$

b) $V_N(\text{MIN}) = 20.4 - 2.74 = 17.66\text{V}$ $I_L = 0.45\text{W}/9 = .05\text{A}$
 $\therefore R_S = (17.66 - 9.0)/.05 \approx 173\Omega$
 $V_R = 0.134 \times 9.0 = 1.21\text{V}$

A-2. (4pts) For the three-phase rectified output (cover sheet) the ripple $V_R/V_P = 0.134$ without capacitance and $V_R/V_P = 1/(6fR_L C)$ with (large) capacitance across the load R_L .

Why is there a 6 in the denominator? _____

E-1 (only if you have time): Bonus questions

(2 pts) What day of the week is today's date one year from today? Thu

(3 pts) How many complete ceiling tiles are in the ECE3424 lab? 298

(2 pts) How many vertices does a regular convex icosahedron have? 12

(2 pts) How many edges does a regular convex icosahedron have? 30

$12 + 20 - 2$

